

VHDL, an Introduction

Egbert Molenkamp
Department of Electrical Engineering, Mathematics and Computer Science
University of Twente
PO Box 217
7500 AE Enschede
the Netherlands
email: e.molenkamp@utwente.nl




Contents

- Problem
- VHDL, the history
- Properties of VHDL
- Alternative VHDL descriptions of the sr latch
- Test Bench
- VHDL Analysis, Elaboration, and Simulation



Moore's Law

 

Janick Bergeron



© 1989-2011 E. Molenkamp, University of Twente, the Netherlands, VHDL: an Introduction

3

Why was VHDL developed (1981) ?

- ➔ Each company uses its own 'language'
 - portability problems.
 - DoD got different descriptions for their VHSIC (Very High Speed Integrated Circuit) program.
- ➔ Reusability not easy
- ➔ Tools from logical level until realization available, but a lack of high level description tools



© 1989-2011 E. Molenkamp, University of Twente, the Netherlands, VHDL: an Introduction

4

History van VHDL

- ➔ June 1981: Woods Hole *Summer Study on Hardware Description Languages* Workshop
- ➔ Aug. 1983: Start of VHDL project
- ➔ Aug. 1985: VHDL version 7.2 (DoD)
- ➔ March 1986: IEEE starts standardization
- ➔ Dec. 1987: Std. 1076-1987
- ➔ June 1990: Preparation rebaloting (P1076-1992/A)
- ➔ Sept. 1993: Std. 1076-1993
- ➔ March 2002: Std. 1076-2002 (major goal: 'bug fix')
- ➔ Sept. 2008: Std. 1076-2008
- ➔ ..

VHSIC Hardware
Description Language



Properties of VHDL

- ➔ Hierarchy supported
- ➔ Support of different design flows
 - top-down
 - bottom-up
 - mixed
- ➔ Technology independent
- ➔ Synchrone / asynchrone models
- ➔ Different description styles supported
 - finite state machine
 - algorithms
 - boolean equations



Properties of VHDL /2

- ➔ Second-sourcing easy
 - CAD /CAE Tool independent
- ➔ Higher level of abstraction
 - Handling complexity
 - Suitable for behavioral until logical level
 - Synthesis tools for the realization
- ➔ Early capture of design faults
- ➔ LSI modeling easy, due to 'components', 'functions', 'procedures' and 'packages'



Properties of VHDL /3

- ➔ No restrictions on the size
- ➔ 'test benches' in the same language > portable!
- ➔ Due to 'generics' backannotation is easy
- ➔ Strongly typed language. User defined types possible.



Demanded by the DoD
An IEEE and ANSI standard




Current use of VHDL

- ➔ Modelling
- ➔ Design flow
 - Designer writes VHDL
 - Intermediate format (VHDL automatically generated)

Synthesis, the mapping to hardware,
is **not** part of the VHDL standard.




schematic capture

 

What is the behavior of this circuit ?




schematic capture /2

 

What is the behavior of this circuit ?



Textual approach

 


```
outp <= '1' WHEN inp > 2 ELSE
      '0';
```

a VHDL statement

What is the behavior of this “circuit” ?



Interface: the ENTITY

 


```
-- author: ....this line is comment
ENTITY greater_2 IS
  PORT ( inp  : IN bit_vector(2 DOWNT0 0);
        outp : OUT bit
      );
END greater_2;
```

Alternatives for the last line:

```
-END;
-END ENTITY greater_2;
```




Body: the ARCHITECTURE

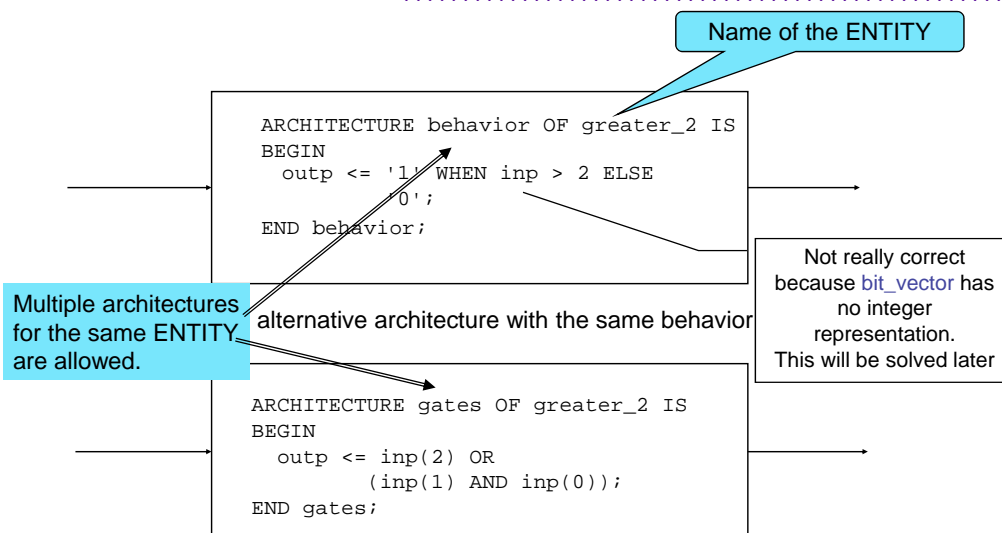

"design units" of VHDL

- ➔ Entity
 - Architecture

 

ARCHITECTURE

```

ARCHITECTURE architecture_name OF entity_name IS....
  Declarations (for local use only!) {
    CONSTANT level : integer := 2;
    SIGNAL a,b,c : bit := '0';      -- initial value is optional
    FUNCTION, PROCEDURE, COMPONENT declarations
  BEGIN
    a <= in1 AND in2;
    b <= in1 OR in2;      -- sensitivity list is implicit
    three concurrent statements {
      PROCESS (a,b)      -- sensitivity list
      VARIABLE loc : bit;
      BEGIN
        loc := a XOR b;
        c <= NOT loc;
      END PROCESS;
    } Sequential statements, also
    END architecture_name;
    if condition then <else> end if;
    case,
    iteration schemes (while, for loop)
    ..

```



Some sequential statements

```
IF a>b THEN
  z <= a;
ELSIF a > c THEN
  z <= b;
  y <= a;
ELSE
  z <= c;
END IF;
```

```
CASE inp IS
  WHEN 0      => statement(s)
  WHEN 1 | 4  => statement(s)
  WHEN OTHERS => statement(s)
END CASE;
```


```
FOR i IN 0 TO 100 LOOP
  y := i * z;
  EXIT WHEN y >= 10;
END LOOP;
```

```
WAIT UNTIL clk='1';
```

Wait until rising edge of signal clk



SR Latch

 

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY sr_latch IS
  PORT (s, r : IN  std_ulogic;
        q, qn : OUT std_ulogic);
END sr_latch;
```



Logical levels in VHDL

Standard:

- In library **Std** type **bit**.
- In library **IEEE** type **std_ulogic**.

MVL9

```
TYPE std_ulogic IS
('U', -- Uninitialized
 'X', -- Forcing Unknown
 '0', -- Forcing 0
 '1', -- Forcing 1
 'Z', -- High Impedance
 'W', -- Weak Unknown
 'L', -- Weak 0
 'H', -- Weak 1
 '-'), -- Don't care
);
```

MVL2

```
TYPE bit IS
('0', -- Forcing 0
 '1', -- Forcing 1
 );
```



SR latch, data flow; (parallelism)

ARCHITECTURE dataflow OF sr_latch IS

SIGNAL qi, qni : std_ulogic;

BEGIN

qi <= r NOR qni AFTER 5 ns;

qni <= s NOR qi AFTER 3 ns;


q <= qi;

qn <= qni;

END dataflow;



not sequential

 

Input/output modes

- ➔ IN only reading of port is allowed
- ➔ OUT only writing to port is allowed
- ➔ INOUT reading of and writing to the port is allowed
- ➔ BUFFER, LINKAGE
 Not part of this course

Do not use mode *inout* if it is not a bidirectional port



SR Latch, structure; (netlist)

ARCHITECTURE structure OF sr_latch IS

```
COMPONENT nor2 IS
  PORT (a,b : IN std_ulogic;
        y  : OUT std_ulogic);
```

```
END COMPONENT;
```

```
SIGNAL qi, qni : std_ulogic;
```

BEGIN

```
n1 : nor2 PORT MAP(r,qni,qi);
```

```
n2 : nor2 PORT MAP(s,qi,qni);
```

```
q <= qi;
```

```
qn <= qni;
```

END structure;

Tip for component declaration:

- Copy corresponding entity declaration
- Change entity name at the end in "COMPONENT"
- Keyword "IS" allowed since VHDL'93)



SR Latch, behaviour; (sequential!)

ARCHITECTURE behaviour OF sr_latch IS

BEGIN

PROCESS(s,r)

BEGIN

IF s='1' AND r='0'

THEN q <='1'; qn<='0';

ELSIF s='0' AND r='1'

THEN q <='0'; qn<='1';


ELSIF s='1' AND r='1'

THEN q <='-'; qn <='-';

END IF;

END PROCESS;

END behaviour;

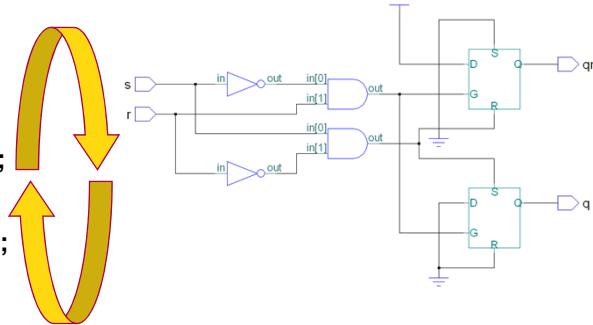

Description styles for architectures

➔ Structure

- Component declarations
- Component instantiations

A "netlist" description!

Error sensitive

Use with care

➔ Data flow

- Concurrent signal assignment statements

Parallelism of hardware

➔ Behaviour

- Process description


Sequential description of the behaviour

Simple!

➔ Mixture allowed



VHDL Analysis

 


Analysis - Compilation without code generation:

- Input: *design file* containing one or more *design units*
- Output: one *library unit* per *design unit*
- Libraries:
 - Resource Libraries: Std, IEEE, ...
 - A single working library: *Work*



Test Bench

 

```
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;  
ENTITY test_bench IS  
    PORT (q,qn : OUT std_ulogic);  
END test_bench;
```



Test Bench /2

ARCHITECTURE structure OF test_bench IS

COMPONENT sr_latch IS

PORT (s, r : IN std_ulogic;

q, qn : OUT std_ulogic);

END COMPONENT;

COMPONENT test_set IS

PORT (set, reset : OUT std_ulogic := '0');

END COMPONENT;

SIGNAL si, ri : std_ulogic;

BEGIN

latch: **sr_latch** **PORT MAP**(si,ri,q,qn);

testb: **test_set** **PORT MAP**(si,ri);

END structure;



© 1989-2011 E. Molenkamp, University of Twente, the Netherlands, VHDL: an Introduction

27

Association list

➤ Positional association:

- testb:test_set PORT MAP(si,ri);

➤ Named association:

- testb:test_set PORT MAP(reset => ri,
set => si);

formal
parameter

actual
parameter



© 1989-2011 E. Molenkamp, University of Twente, the Netherlands, VHDL: an Introduction

28

Test Bench /3

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY test_set IS
    PORT (set, reset : OUT std_ulogic := '0');
END test_set;
```

```
ARCHITECTURE TestSet1 OF test_set IS
    SIGNAL rs : std_ulogic_vector(1 DOWNTO 0) := "00";
BEGIN
    rs <= "01" AFTER 50 ns,
        "00" AFTER 100 ns,
        "10" AFTER 150 ns,
        "00" AFTER 200 ns;
    reset <= rs(1);
    set <= rs(0);
END TestSet1;
```



Test Bench /4

Still problems left:


- Which *architecture* is tested?
- Manual verification of the simulation results is error prone.

content of library WORK
<entity> (<architecture>)

- sr_latch (dataflow)
- sr_latch (structure)
- sr_latch (behaviour)
- test_bench (structure)
- test_set (TestSet1)



Simulation

 

Elaboration

- **depends on the selected design entity to simulate/synthesize**
- **signals are created**
signals are not created/removed in the execution phase
- **components instantiated**
design entities are bound
- **initial values are assigned to objects**



SR latch, order of statements

ARCHITECTURE exa1 OF sr_latch IS

SIGNAL qi, qni : std_ulogic;

BEGIN

qi <= r NOR qni;

qni <= s NOR qi;

q <= qi;

qn <= qni;

END exa1;

ARCHITECTURE exa2 OF sr_latch IS

SIGNAL qi, qni : std_ulogic;

BEGIN

qni <= s NOR qi;

qi <= r NOR qni;

q <= qi;

qn <= qni;

END exa2;

Both descriptions have the same behaviour?




Delta delay

Delta delay makes:

- ➔ **Order independent descriptions possible**
- ➔ **Ensures that a circuit is stable before time advances**
 - Any number of deltas < 1 fs
 - **Delta delayed oscillators possible**
No progress in time, hence also waveform display does not show any progress
 - **Most tools can set an upper limit on the number deltas**



Simulation cycle

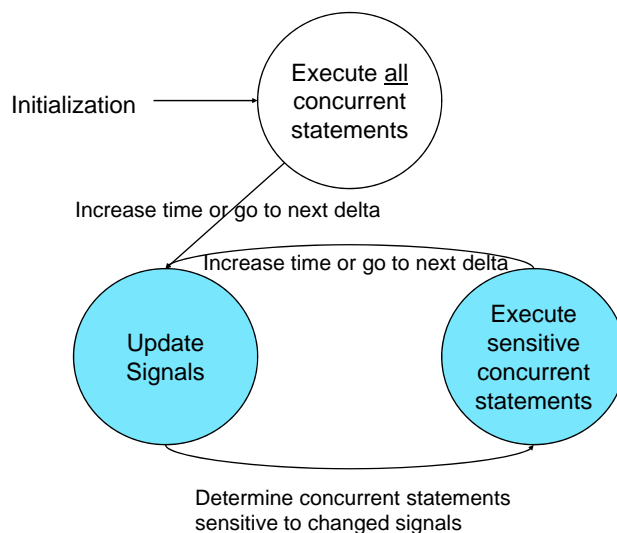

Simulation cycle /2

A: $qi \leq r \text{ NOR } qni$;

D: $q \leq qi$;

B: $qn \leq qni$;

C: $qni \leq s \text{ NOR } qi$;


time	s	r	qi	qni	q	qn
t1	1	1	0	0	0	0
t2	0	0	0	0	0	0
processes A and C are sensitive						
t2+1δ	0	0	1	1	0	0
processes A, B, C and D are sensitive						
t2+2δ	0	0	0	0	1	1
t2+3δ	0	0	1	1	0	0
t2+4δ	0	0	0	0	1	1



© 1989-2011 E. Molenkamp, University of Twente, the Netherlands, VHDL: an Introduction

35

Simulation cycle /3

 

$qi \leq r \text{ NOR } qni$ AFTER 3 ns;


$qni \leq s \text{ NOR } qi$ AFTER 3 ns;



© 1989-2011 E. Molenkamp, University of Twente, the Netherlands, VHDL: an Introduction

36

Simulation cycle /4

 

$qi \leq r \text{ NOR } qni \text{ AFTER } 3 \text{ ns};$

$qni \leq s \text{ NOR } qi \text{ AFTER } 5 \text{ ns};$



Variables, Signals, and Constants

variable is updated immediately

signal is updated **after** a DELTA delay, hence the next statements will use the 'old' value!

sig1 is not yet updated here!

```
label_optional:PROCESS
  VARIABLE var : std_ulogic;
  CONSTANT high : std_ulogic := '1';
  BEGIN
    var := a NOR b;
    sig1 <= var AND high;
    sig2 <= NOT sig1;
    WAIT ON a,b,sig1;
  END PROCESS label_optional;
```



Remember this!

Assignments to

- variables:
 - **:=** as assignment operator
 - always immediately
- signals
 - **<=** as assignment operator
 - at least after a *delta delay*



Simulation cycle /3

Which behavior is exactly the same?

(The signals *inp* and *outp* are the only signals in the port declaration of the entity. Other signals are declared locally.)

```
A:PROCESS (inp)
  VARIABLE v : bit;
BEGIN
  v := inp;
  outp <= v;
END PROCESS;
```

```
B:PROCESS (inp)
BEGIN
  s <= inp;
  outp <= s;
END PROCESS;
```

```
C:PROCESS (inp,s)
BEGIN
  outp <= s;
  s <= inp;
END PROCESS;
```

```
D: outp <= inp;
```

```
E:PROCESS (inp)
  VARIABLE v : bit;
BEGIN
  outp <= v;
  v :=inp;
END PROCESS;
```

```
F:PROCESS (inp,s)
BEGIN
  s <= inp;
  outp <= s;
END PROCESS;
```



Summary: VHDL is Concurrent and Sequential

- ⇒ Statements in architecture are *concurrently* executed
 - The ordering in the design file is not important.
 - Concurrent statements communicate via *signals*.
 - Signals are declared at process level (not *in* a process).
 - An assignment to a signal will at least update the value of that signal after one delta delay.
 - Communication is also possible via *shared variables* (Std. 1076-1993). But not portable anymore!
- ⇒ A process is internally executed *sequentially*
 - Variables may only be declared in sequential part, e.g. in the declaration region of a process.
 - An assignment to a variable always immediately updates the value.

