 


behavior → algorithm → datapath & controller

Processor

1


Global design flow



Processor

2


Processor: datapath & controller

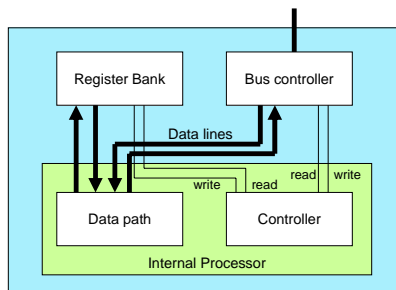

Processor

3

Test environment: verification

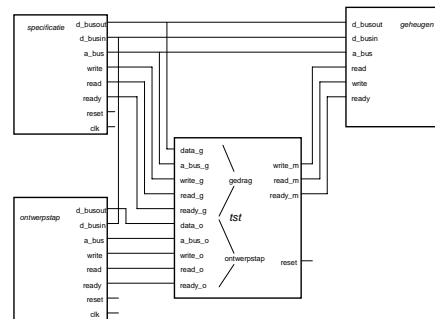

Processor

4

Multiplier: Behavior

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
ENTITY multiply IS
    GENERIC (width : integer := 4);
    PORT (op1, op2 : IN unsigned(width-1 DOWNTO 0);
          result : OUT unsigned(2*width-1 DOWNTO 0));
END multiply;
    
```

```


ARCHITECTURE behaviour OF multiply IS
BEGIN
    result <= op1 * op2;
END behaviour;
    
```

Notice that:

- no implementation details are given
- description is readable

Processor


5

 

Processor

6

Algorithm: shift-add

 

Processor

7

Algorithm: shift_add


```

ARCHITECTURE algorithm OF multiply IS
BEGIN
  PROCESS(op1,op2)
  VARIABLE r1,r2,r3 : unsigned(width-1 DOWNTO 0);
  VARIABLE co : std_ulogic;
  VARIABLE s : unsigned(width DOWNTO 0);
  CONSTANT zero: unsigned(width-1 DOWNTO 0):=(OTHERS =>'0');
  BEGIN
    r1:=op1;
    r2:=op2;
    -- initialize r3 met all '0'
    r3:= (OTHERS =>'0');
    -- repeat add-shift
    FOR i IN 1 TO width LOOP
      CASE r2(i) IS
        WHEN '1' => s:= resize(r3,width+1) + r1;
        WHEN OTHERS => s:= resize(r3,width+1);
      END CASE;
      -- shift
      r3:=s(s'LEFT DOWNTO 1);
      r2:=s(0) & r2(r2'LEFT DOWNTO 1);
    END LOOP;
    result <= r3 & r2;
  END PROCESS;
END algorithm;
  
```

Not as readable as the behavioral description,
but the purpose of an algorithm is different!

Processor


8

 

Processor

9

Separation in data path and controller

 


FSM of controller (incomplete)

Processor

10

Interconnection data path and controller

 

Requirements control vector

- description should be readable
- changes in the number and names of control lines should be easy
- no (implicit) coding of control lines
- all control lines should assigned to in a next state

Processor

11

Communication

PORT (c1, c2, c3... : bit;

Controller:
c1 <= '1'; c2 <= '0'; ...

Data path:
IF c1='1' THEN ...

- readable(?)
- not easy to change
- are all control signals assigned a new value?

PORT (c : bit_vector(1 TO n)

Controller:
C(1) <= '1'; c(2) <= '0'; ...

Data path:
IF c(1)='1' THEN ...

- not readable
- error prone
- not easy to change
- all control signals are assigned a value.

Processor

12

Communication: solution

Package control_names, user defined!


```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
PACKAGE control_names IS
  TYPE control_signals IS
    (init, shift, load, en_r1, en_r2, en_r3, en_res);
  -- do not change the following type declaration
  TYPE control_bus IS ARRAY (control_signals) OF std_logic;
END control_names;
```

```
ctrl : control_bus
Examples:
ctrl <= (OTHERS => '0');
ctrl <= (init => '1', OTHERS => '0');
ctrl <= (init | shift => '1', OTHERS => '0');
```

Used in the entity declaration

Processor 13

Data path with gates & VHDL descriptions

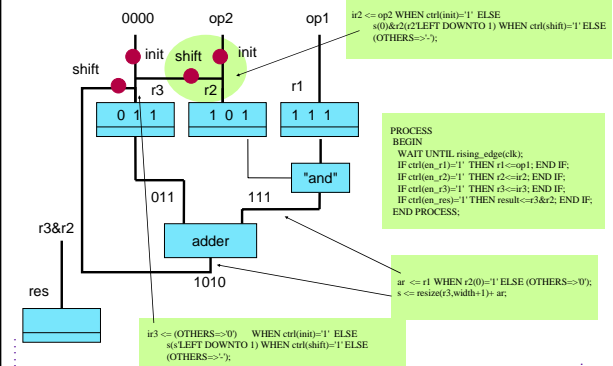

Processor 14

Datapath

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
USE work.control_names.ALL;
ENTITY datapath IS
  GENERIC (width : integer := 4);
  PORT (clk : IN std_logic;
        rst : IN std_logic;
        ctrl : IN control_bus;
        op1, op2 : IN unsigned(width-1 DOWNT0 0);
        result : OUT unsigned(2*width-1 DOWNT0 0));
END datapath;
```

Processor 15

Datapath

```
ARCHITECTURE RTL OF datapath IS
  SIGNAL ir2,ir3,ar,r1,r2,r3 : unsigned(width-1 DOWNT0 0);
  SIGNAL s : unsigned(width DOWNT0 0);
BEGIN
  ir2 <= op2 WHEN ctrl(init)='1' ELSE
    s(0)&r2(r2'LEFT DOWNT0 1) WHEN ctrl(shift)='1' ELSE
    (OTHERS=>'0');

  ir3 <= (OTHERS=>'0') WHEN ctrl(init)='1' ELSE
    s(s'LEFT DOWNT0 1) WHEN ctrl(shift)='1' ELSE
    (OTHERS=>'0');


  ar <= r1 WHEN r2(0)='1' ELSE (OTHERS=>'0');
  s <= resize(r3,width+1)+ ar;

  PROCESS
  BEGIN
    WAIT UNTIL rising_edge(clk);
    IF ctrl(en_r1)='1' THEN r1<=op1; END IF;
    IF ctrl(en_r2)='1' THEN r2<=ir2; END IF;
    IF ctrl(en_r3)='1' THEN r3<=ir3; END IF;
    IF ctrl(en_res)='1' THEN result<=r3&r2; END IF;
  END PROCESS;

END RTL;
```

Processor 16

Datapath

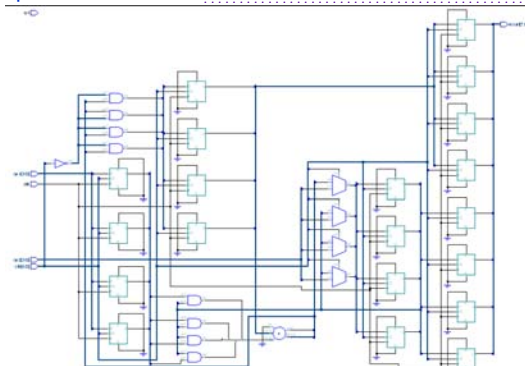

Processor 17

Controller: behavior

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
USE work.control_names.ALL;
ENTITY controller IS
  GENERIC (width : integer := 4);
  PORT (clk : IN std_logic;
        rst : IN std_logic;
        ctrl : OUT control_bus);
END controller;
```

```
ARCHITECTURE behaviour OF controller IS
  BEGIN
  PROCESS
  BEGIN
    reset_lp: LOOP
      -- reset
      ctrl <= (en_r1|en_r2|en_r3|init|en_res => '1', OTHERS => '0');
      WAIT UNTIL rising_edge(clk);
      EXIT WHEN rst='1';
      FOR i IN 1 TO width LOOP
        ctrl <= (en_r2|en_r3|shift=>'1', OTHERS=>'0');
        WAIT UNTIL clk='1';
        EXIT WHEN rst='1';
      END LOOP;
    END PROCESS;
  END behaviour;
```

Processor 18